

CS M51A and EE M16 Summer 2016 Section 1

Logic Design of Digital Systems

Dr. Yutao He

Project #1 - Orientation of Verilog and Vivado

Due: Sunday, July 17th 2016

Name: _____
 Liu Jerry
 Last First

Student ID: _____
 404474229

Discussion: _____
 1A

Date: _____
 07/16/2016

Result	
Correctness	
Creativity	
Report	
Total Score	

Project 1 Report, Title Page Above

Jerry Liu, 404474229

July 16, 2016

2 Project Requirement

In this project, we will use the Xilinx Vivado software and Verilog to implement the circuit that is specified in Figure 1.

Inputs: We have three inputs: x_2, x_1, x_0 , with $x_i \in \{0, 1\}$.

Outputs: We have one output: z , with $z \in \{0, 1\}$.

Function: The canonical form of the output function is

$$z(x_2, x_1, x_0) = \sum m(1, 2, 6) = x'_2x'_1x_0 + x'_2x_1x'_0 + x_2x_1x'_0 = x'_2x'_1x_0 + x_1x'_0$$

3 The Function of The Circuit

In this implementation, we use the sum of minterms. The canonical switching expression is:

$$z(x_2, x_1, x_0) = \sum m(1, 2, 6) = x'_2x'_1x_0 + x'_2x_1x'_0 + x_2x_1x'_0$$

But we can simplify the function to be:

$$z(x_2, x_1, x_0) = x'_2x'_1x_0 + (x'_2 + x_2)x_1x'_0 = x'_2x'_1x_0 + x_1x'_0$$

Let $\text{prod1} = x'_2x'_1x_0$, $\text{prod2} = x_1x'_0$. The corresponding diagram is shown in Figure 1:

 


Figure 1: Schematic Diagram

4 Verilog File

4.1 Circuit Implementation

csm51a_proj1.v

```
module csm51a_proj1(
    input x0,
    input x1,
    input x2,
    output z
);
    // Outputs from NOT and AND gates
    wire x0_not, x1_not, x2_not, prod1, prod2;

    // NOT inputs
    not n1(x0_not, x0);
    not n2(x1_not, x1);
    not n3(x2_not, x2);

    // Calculate Products

    // prod1 = x2'x1'x0
    and a1(prod1, x2_not, x1_not, x0);

    // prod2 = x1x0'
    and a2(prod2, x1, x0_not);

    // Calculate Sum of Products

    // z = prod1 + prod2
    or o1(z, prod1, prod2);

endmodule
```

4.2 Testbench

csm51a_proj1_tb.v

```
module csm51a_proj1_tb(
    output z
);
    // 4-bit integer to avoid overflow from 3-bit integers
    reg [3:0] i;
    // Input variables
    reg x0, x1, x2;

    // Test out implementation
    csm51a_proj1 p1(.z(z), .x0(x0), .x1(x1), .x2(x2));
endmodule
```

```

initial
begin
  for (i = 0; i < 8; i = i + 1)
  begin
    // assign each bit separately
    {x2, x1, x0} = i;
    // delay
    #10;
  end
  $finish;
end
endmodule

```

5 Simulation Result

Here we want to construct and test all possible cases in the truth table: Table 1.

x_2	x_1	x_0	z	m_i
0	0	0	0	m_0
0	0	1	1	m_1
0	1	0	1	m_2
0	1	1	0	m_3
1	0	0	0	m_4
1	0	1	0	m_5
1	1	0	1	m_6
1	1	1	0	m_7

Table 1: Truth Table of the Function

The results are shown clearly in the Figure 2:

 


Figure 2: Screenshot of the Simulation Result

As we can see, the output $z = 1$ if and only if the inputs $(x_2, x_1, x_0) = (0, 0, 1), (0, 1, 0), (1, 1, 0)$ (Corresponding to $i = 1, 2, 6$). This is exactly what we get from the truth table: Table 1.

Note that green regions correspond to the time for a specific variable to have value 1, and for each variable, its value variations are represented on the same line as the variable.

In Figure 3, we can get a more detailed view of variable's values when $z = 1$.

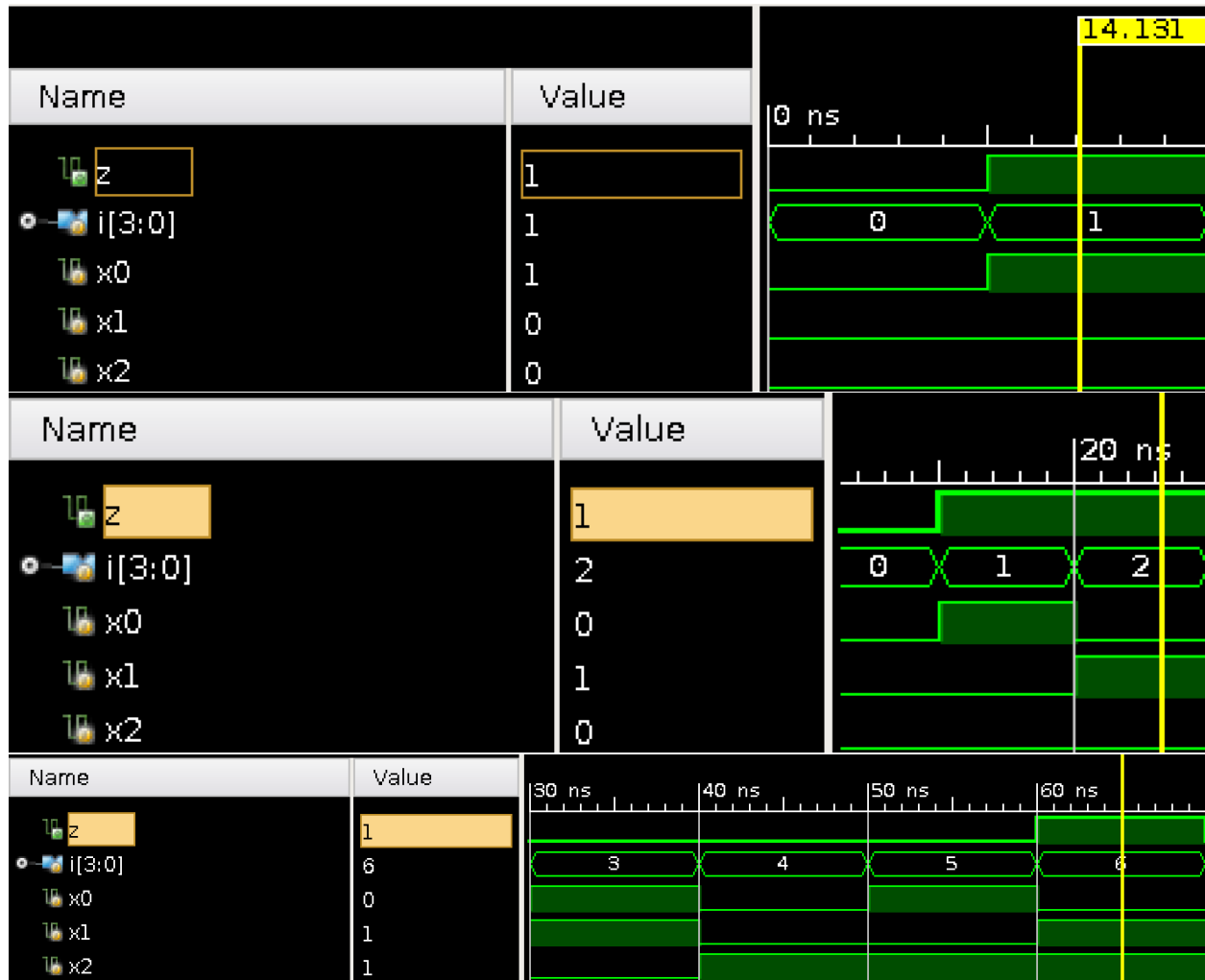


Figure 3: Screenshot of the Simulation Result for Minterms m_1, m_2, m_6

6 The Summary

6.1 Issues Encountered

I tried to implement a *for loop* to run the TestBench, but I had a hard time figuring that out. I asked my TA about it and I was then able to figure out that I need to add a semi-colon in the delay. This is different inside for loops.